

#### Signals & Systems EGE 311-01

Dr. Julio Gonzalez


December 10, 2024

Name	Major
John Urban Quezada	EE
Columbus Enslen	CE


**Design objective:** To design a filter whose output signal will have a desired signal to noise ratio of 50 / 1.
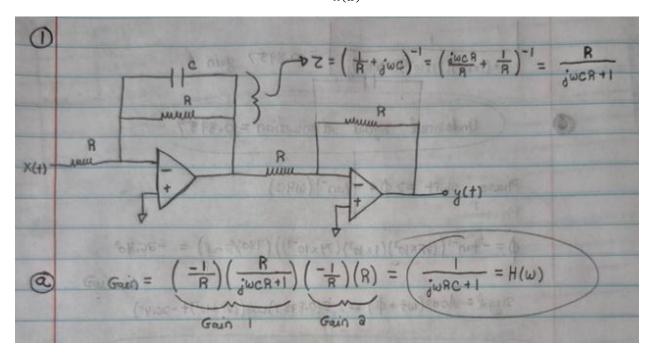
# **Part 1: First-Order Filter:**


**Step 1:** Finding the transfer function  $H(\omega) = \frac{Y(\omega)}{X(\omega)}$ 



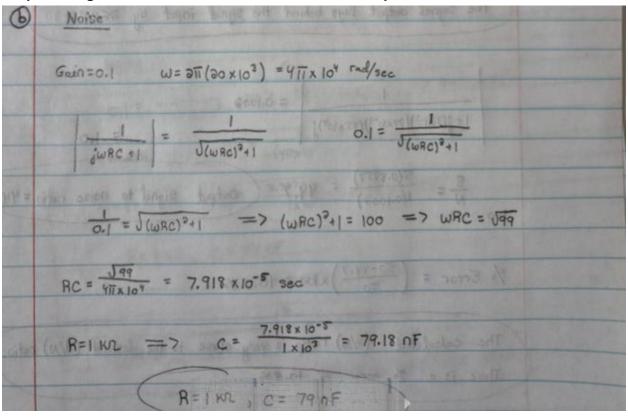Step 2: Design the filter so that it attenuates the noise by a factor of 10



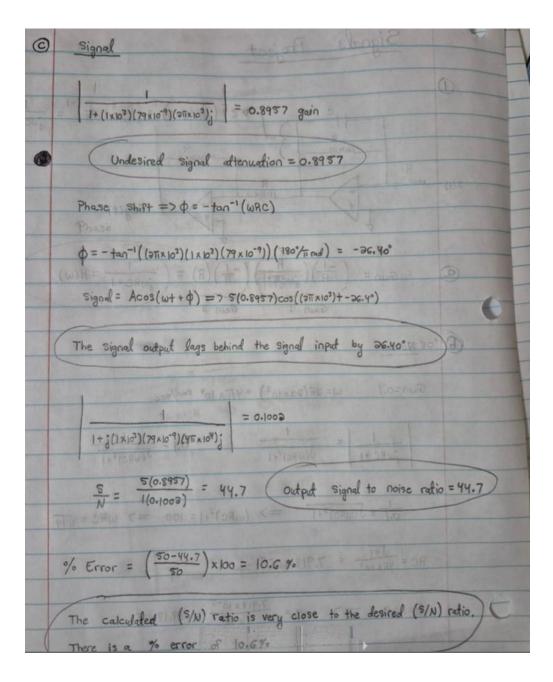**Step 3:** After simulating the designed circuit, we can see that the filter does severely affect the noise. However, there are some side effects such as a phase shift and signal attenuation



Undesired Attenuation: 0.8957 Signal to Noise Ratio (S/N): 44.7

Phase Shift: 26.4°

**NOTE:** The signal to noise ratio is 10.6% lower than our desired ratio of 50.

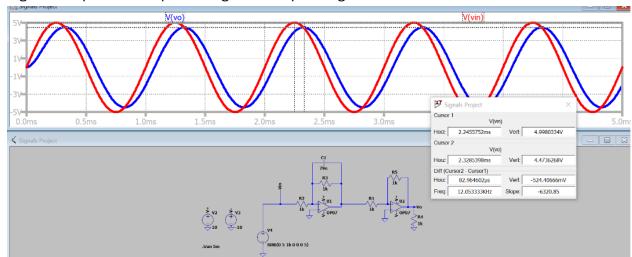


Figure 1: Input and output voltages of the pure signal

Figure 1: Input and output voltages of the pure signal

**NOTE:** The simulation demonstrates the slight phase 26.4° and the signal attenuation of 0.8957.

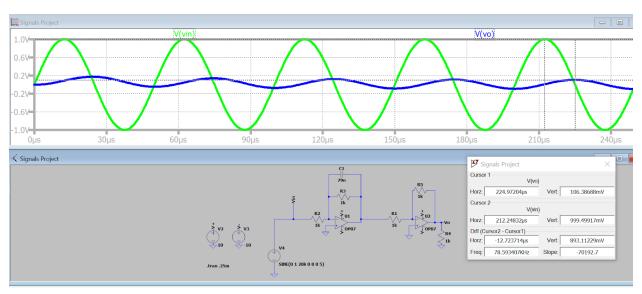


Figure 2: Input and output voltages of the pure noise

**NOTE:** The simulation demonstrates the filter's ability to reduce the noise by a factor of nearly 10.


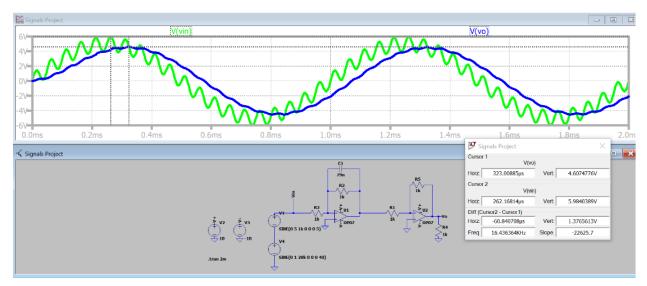


Figure 3: Input and output voltages of the signal plus the noise


**NOTE:** The simulation shows the filter's ability to maintain the desired signal and filter out the high frequency noise.
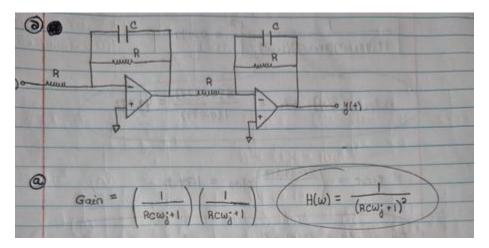
# Part 2: Second-Order Filter


**Step 1:** Finding the transfer function  $H(\omega) = \frac{Y(\omega)}{X(\omega)}$ 




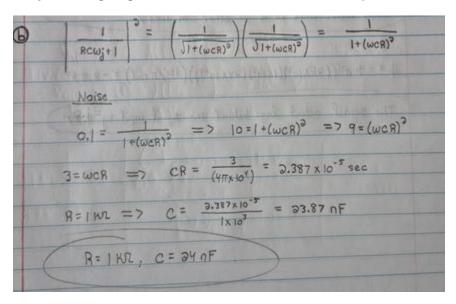Step 2: Designing the filter to attenuate the noise by a factor of 10



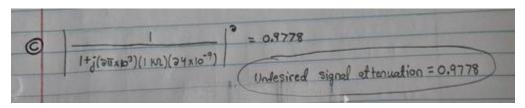**Step 3:** Calculating the side effects of the filter



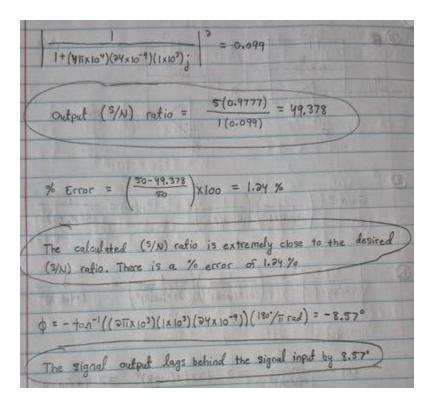

Undesired Attenuation: 0.9778 Signal to Noise Ratio (S/N): 49.378

Phase Shift: 8.57°

**NOTE:** The calculated Signal to Noise ratio (S/N) is extremely close to the desired ratio of 50. There is a percent error of 1.24% between the desired and calculated error.

## Step 4: Simulations

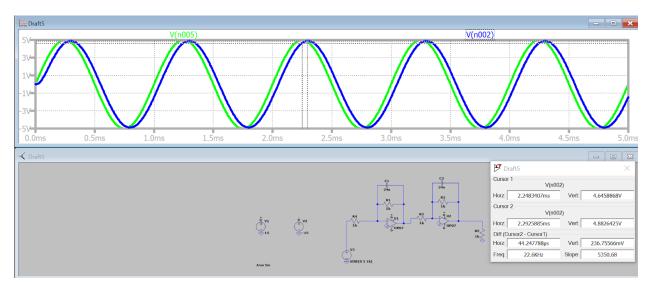


Figure 4: Input and output of the pure signal

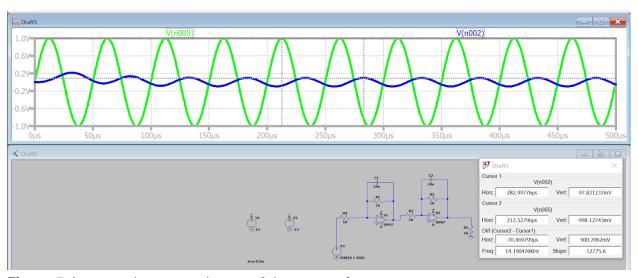


Figure 5: Input and output voltages of the pure noise

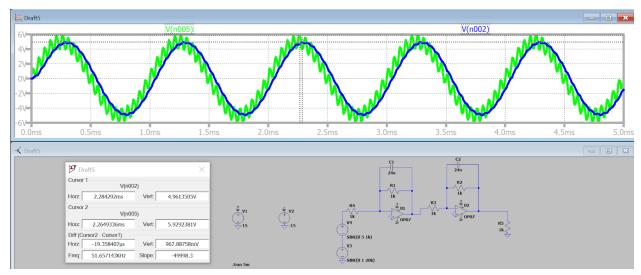


Figure 6: Input and output voltages of the signal plus the noise

## Part 3: Comparison of the two filters

The first order-filter was able to achieve a signal to noise ratio (S/N) of 44.7. With a percent error of 10.6%. Our second-order filter, however achieved a signal to noise ratio (S/N) of 49.4. This was much closer to our goal of 50 with only a 1.24% percent error.

There are two main side effects of our filters. Undesired Attenuation and a phase shift of the output signal. The undesired attenuation for both signals is a slight, diminishing gain in the output. The closer the undesired attenuation is to 1 the better the filter.

The first-order filter had an undesired attenuation of 0.8957 and a phase shift of 26.4°. The undesired attenuation of our first-order filter created a noticeable change in amplitude to our output signal. The filter has a percent error of 0.209% compared to our goal of 1. Dependent on the application the attenuation may not be a problem. However, the resulting phase shift of the first-order filter is more noticeable, causing a substantial delay in the output. Limiting the filters application in applications that require faster responses.

The second-order filter had an undesired attenuation of 0.9788 and a phase shift of 8.57°. This undesired attenuation is much closer to 1 with a percent error of 0.044%. This second-order filter is much more exact with an undesired attenuation equal to 1 and a much smaller phase shift closer to 0.

In conclusion the second-order filter, when compared to the first-order filter, is much more exact. The second-order filter produces a signal to noise ratio closer to our desired 50/1,

while also having an undesired attenuation closer to one and a phase shift closer to 0. The first-order filter however is still relevant as it only requires a single capacitor instead of two. Meaning the cost of production for the first-order filter should be lower. So, depending on your application, the first-order filter still has its place.